

Roll No.

Exam Code : J-19

Subject Code—0379

M.C.A. (Second Year) EXAMINATION

(5 Years Integrated Course)

(Main & Re-appear for Batch 2009 Onwards)

DIGITAL ELECTRONICS

MCA-203

Time : 3 Hours

Maximum Marks : 70

Section A

Note : Attempt any *Seven* questions. **7×5=35**

1. List the steps to convert a decimal number to an octal number.
2. What are Parity ? How can it be detected and corrected ?
3. Draw and explain 8 : 1 multiplexer.

(2-67-1-0519) **J-0379**

P.T.O.

4. Differentiate between minterms and maxterms.
What are their uses ?
5. Draw excitation table for a JK flip-flop and explain its behaviour.
6. Draw and explain serial in serial out shift register.
7. Design a mod-7 ripple counter.
8. Draw circuit for a Tri-state logic. How does it work ?
9. Draw a TTL NAND gate. How does it work ?
10. Draw a full adder circuit. How does it work ?

Section B

Note : Attempt all the questions.

11. What are universal gates ? How we can design other gates with NOR gates ? 12

Or

Explain the various logic families and compare their features.

12. Design :

$$f(A, B, C, D) = \pi(0, 2, 4, 6, 9, 10) + \phi(11, 13)$$

with NOR gates only. 12

Or

Design a decade counter by using JK flip-flops.

13. What are universal shift register ? Draw circuit and explain its behaviour. 11

Or

What are ASCII codes ? What are their applications ?